

**TDC Odd Semester Exam., 2020
held in July, 2021**

COMPUTER APPLICATION
(Honours)

(1st Semester)

Course No. : BCAC-101

(Digital Logic)

Full Marks : 35

Pass Marks : 12

Time : 2 hours

*The figures in the margin indicate full marks
for the questions*

Answer **five** questions, selecting **one** from each Unit

UNIT—I

1. (a) Write short notes on TTL and ECL. 4
(b) Explain the characteristics of digital ICs. 3
2. What is multivibrator? Briefly explain the different types of multivibrator. 7

UNIT—II

3. (a) Express the following Boolean function in sum of minterms : 4
 $f(x, y, z) = x + y'z$
- (b) Simplify the following : 3
 $F(A, B, C) = (2, 3, 6, 7)$
4. (a) Draw Karnaugh map and simplify the following Boolean expressions : 4
(i) $AB + \bar{A}\bar{B}$
(ii) $ABC + \bar{A}B\bar{C} + A\bar{B}C + \bar{A}\bar{B}C$
- (b) Convert $(10010110)_2$ to decimal, octal and hexadecimal numbers. 3

UNIT—III

5. (a) Design a 2 to 4 line decoder with enable input. 4
(b) Draw the logic diagram and function table of a 4 to 1 line multiplexer. 3
6. Design a 4-bit binary adder-subtractor with explanation of full adder. 7

(3)

UNIT—IV

7. (a) What is sequential circuit? How does it differ from combinational circuit? 2
(b) Explain *D* flip-flop and *T* flip-flop. 5
8. (a) Explain *R-S* flip-flop. 4
(b) Obtain the excitation table of *J-K* flip-flop. 3

UNIT—V

9. Explain the working principle of a binary ripple counter. 7
10. Write short notes on the following : $3\frac{1}{2}+3\frac{1}{2}=7$
(a) Synchronous counter
(b) Random Access Memory

★ ★ ★