

2020/TDC/ODD/SEM/  
BCSP-101/197

( 2 )

TDC Odd Semester Exam., 2020  
held in July, 2021

COMPUTER SCIENCE

( Pass )

( 1st Semester )

Course No. : BCSP-101

( Digital Electronics, Computer Fundamentals  
and Computer System Architecture )

Full Marks : 35  
Pass Marks : 12

Time : 2 hours

The figures in the margin indicate full marks  
for the questions

Answer **five** questions, taking **one** from each Unit

UNIT—I

1. Explain the characteristics of digital integrated circuits. 7
2. Given the following Boolean function :  
 $F = ABC + \overline{BCD} + \overline{ABC}$   
(a) Obtain the truth table of the function.

10-21/500

( Turn Over )

- (b) Simplify the function to a minimum number of literals.
- (c) Realize the function  $F$  using NAND gate. 2+2+3=7

UNIT—II

3. (a) Write short notes on the following : 1½×2=3  
(i) Shift register  
(ii) Ripple counter  
(b) Explain R-S flip-flop. Compare it with J-K flip-flop. 4
4. (a) What is multiplexer? 2  
(b) Implement the following Boolean function by using an 8 1 multiplexer : 5  
 $F(A, B, C, D) = m(0, 3, 5, 6, 9, 10, 12, 15)$

UNIT—III

5. (a) What is register transfer language? 3  
(b) Explain an ALU. 4
6. (a) What are interrupts? 3  
(b) What are program counters, instruction register, address register and data register? 4

10-21/500

( Continued )

( 3 )

UNIT—IV

7. Explain CPU organization with example. 7
8. (a) Explain the functions of CPU registers. 4  
(b) What are the major attributes of RISC computers? 3

UNIT—V

9. Explain with neat diagram the functions of a DMA controller. 7
10. (a) What is priority interrupt? 2  
(b) Explain cache memory and virtual memory. 5

\*\*\*